
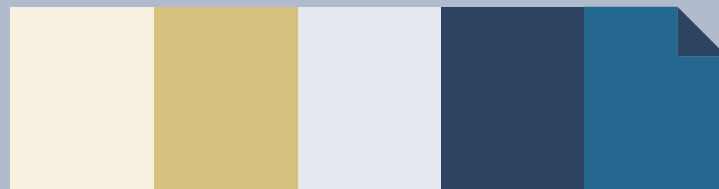


Brief Contents

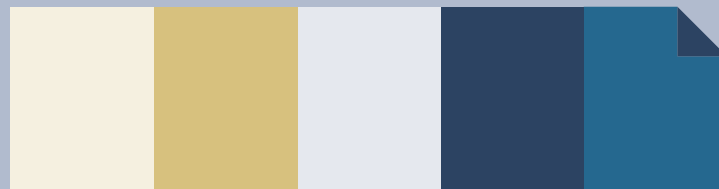

Chapter 1	Circuit Terminology	1	Chapter 10	Laplace Transform Analysis Technique	466
Chapter 2	Resistive Circuits	33	Chapter 11	Fourier Analysis Technique	520
Chapter 3	Analysis Techniques	82	Appendix A	Symbols, Quantities, and Units	575
Chapter 4	Operational Amplifiers	130	Appendix B	Solving Simultaneous Equations	577
Chapter 5	RC and RL First-Order Circuits	181	Appendix C	Overview of Multisim	581
Chapter 6	RLC Circuits	247	Appendix D	Mathematical Formulas	585
Chapter 7	ac Analysis	300	Appendix E	Answers to Selected Problems	588
Chapter 8	ac Power	368	Index		591
Chapter 9	Frequency Response of Circuits and Filters	404			

Contents



Preface

xiii

Chapter 1 Circuit Terminology

1

	Cell-Phone Circuit Architecture	2
1-1	Historical Timeline	3
1-2	Units, Dimensions, and Notation	9
TB1	Micro- and Nanotechnology	10
1-3	Electric Charge and Current	13
1-4	Voltage and Power	17
TB2	Moore's Law and Scaling	20
1-5	Circuit Elements	23
	Chapter 1 Relationships	28
	Chapter Highlights	28
	Glossary of Important Terms	29
	Problems	29

Chapter 2 Resistive Circuits

33

	Overview	34
2-1	Ohm's Law	34
TB3	Superconductivity	38
2-2	Circuit Topology	40
2-3	Kirchhoff's Law	43
2-4	Equivalent Circuits	48
TB4	Resistors as Sensors	56
2-5	Wye–Delta ($Y-\Delta$) Transformation	58

2-6	The Wheatstone Bridge	61
2-7	Application Note: Linear versus Nonlinear $i-v$ Relationships	62
2-8	Introducing Multisim	66
	Chapter 2 Relationships	73
	Chapter Highlights	73
	Glossary of Important Terms	74
	Problems	74

Chapter 3 Analysis Techniques

82

	Overview	83
3-1	Node-Voltage Method	83
3-2	Mesh-Current Method	88
3-3	By-Inspection Methods	92
TB5	Light-Emitting Diodes (LEDs)	96
3-4	Source Superposition	97
3-5	Thévenin and Norton Equivalent Circuits	98
TB6	Display Technologies	106
3-6	Maximum Power Transfer	110
3-7	Application Note: Bipolar Junction Transistor (BJT)	111
3-8	Nodal Analysis with Multisim	114
	Chapter 3 Relationships	117
	Chapter Highlights	118
	Glossary of Important Terms	118
	Problems	119

Chapter 4 Operational Amplifiers 130

Overview	131
4-1 Op-Amp Characteristics	131
TB7 Integrated Circuit Fabrication Process	135
4-2 Negative Feedback	139
4-3 Ideal Op-Amp Model	140
4-4 Inverting Amplifier	142
4-5 Summing Amplifier	144
4-6 Difference Amplifier	147
4-7 Voltage Follower	148
4-8 Op-Amp Signal-Processing Circuits	149
4-9 Instrumentation Amplifier	152
4-10 Digital-to-Analog Converters (DAC)	154
4-11 The MOSFET as a Voltage-Controlled Current Source	156
TB8 The Electromagnetic Spectrum	158
TB9 Computer Memory Circuits	163
4-12 Application Note: Neural Probes	166
4-13 Multisim Analysis	168
Chapter 4 Relationships	172
Chapter Highlights	173
Glossary of Important Terms	173
Problems	173

Chapter 5 RC and RL First-Order Circuits 181

Overview	182
5-1 Nonperiodic Waveforms	183
5-2 Capacitors	189
TB10 Flash Memory	190
TB11 Supercapacitors	199
5-3 Inductors	202
5-4 Response of the RC Circuit	208
5-5 Response of the RL Circuit	216
5-6 RC Op-Amp Circuits	221
5-7 Application Note: Parasitic Capacitance and Computer Processor Speed	226
5-8 Analyzing Circuit Response with Multisim	231
Chapter 5 Relationships	234
Chapter Highlights	235
Glossary of Important Terms	235
Problems	236

Chapter 6 RLC Circuits 247

Overview	248
6-1 Initial and Final Conditions	248
6-2 General Solution	253

6-3 Natural Response of the Series RLC Circuit	254
6-4 Total Response of the Series RLC Circuit	261
TB12 Micromechanical Sensors and Actuators	269
6-5 The Parallel RLC Circuit	273
6-6 General Solution for Any Second-Order Circuit	275
6-7 Application Note: Micromechanical Transducers	282
6-8 Multisim Analysis of Circuit Response	284
TB13 Touchscreens and Active Digitizers	289
Chapter 6 Relationships	292
Chapter Highlights	292
Glossary of Important Terms	292
Problems	292

Chapter 7 ac Analysis 300

Overview	301
7-1 Sinusoidal Signals	301
7-2 Review of Complex Numbers	304
7-3 Phasor Domain	307
TB14 Noise-Cancellation Headphones	308
7-4 Phasor-Domain Analysis	315
7-5 Impedance Transformations	318
7-6 Equivalent Circuits	324
TB15 Night-Vision Goggles	325
7-7 Phasor Diagrams	330
7-8 Phase-Shift Circuits	333
7-9 Phasor-Domain Analysis Techniques	336
TB16 Crystal Oscillators	343
7-10 Application Note: Power-Supply Circuits	346
7-11 Multisim Analysis of ac Circuits	351
Chapter 7 Relationships	357
Chapter Highlights	357
Glossary of Important Terms	358
Problems	358

Chapter 8 ac Power 368

Overview	369
8-1 Periodic Waveforms	369
8-2 Average Power	372
8-3 Complex Power	374
8-4 The Power Factor	378
8-5 Maximum Power Transfer	383
TB17 Bandwidth, Data Rate, and Communication	384

8-6	Application Note: Three-Phase Circuits	388	TB21	Hard Disk Drives (HDD)	509
8-7	Measuring Power With Multisim	392		Chapter 10 Relationships	511
	Chapter 8 Relationships	395		Chapter Highlights	511
	Chapter Highlights	395		Glossary of Important Terms	512
	Glossary of Important Terms	396		Problems	512
	Problems	396			
Putting it All Together		461			
Chapter 9 Frequency Response of Circuits and Filters		404	Chapter 11 Fourier Analysis Technique		
	Overview	405		Overview	521
9-1	The Transfer Function	405	11-1	Fourier Series Analysis Technique	521
9-2	Scaling	410	11-2	Fourier Series Representation	523
9-3	Bode Plots	412	11-3	Circuit Applications	533
9-4	Passive Filters	422	TB22	Synthetic Biology	536
9-5	Filter Order	430	11-4	Average Power	539
9-6	Active Filters	433	11-5	Fourier Transform	540
TB18	Electrical Engineering and the Audiophile	435	11-6	Fourier Transform Pairs	545
9-7	Cascaded Active Filters	438	TB23	Mapping the Entire World in 3-D	551
TB19	Smart Dust, Sensor Webs, and Ubiquitous Computing	442	11-7	Fourier versus Laplace	554
9-8	Application Note: Modulation and the Superheterodyne Receiver	445	11-8	Circuit Analysis with Fourier Transform	554
9-9	Spectral Response with Multisim	448	11-9	Application Note: Phase Information	556
	Chapter 9 Relationships	452	11-10	Multisim: Mixed-Signal Circuits and the Sigma-Delta Modulator	561
	Chapter Highlights	453		Chapter 11 Relationships	566
	Glossary of Important Terms	453		Chapter Highlights	566
	Problems	453		Glossary of Important Terms	566
				Problems	567
Chapter 10 Laplace Transform Analysis Technique		466	Appendix A Symbols, Quantities, and Units		
	Overview	467	575		
10-1	Singularity Functions	467	Appendix B Solving Simultaneous Equations		
10-2	Definition of the Laplace Transform	470	577		
10-3	Properties of the Laplace Transform	473	Appendix C Overview of Multisim		
10-4	Circuit Analysis Procedure	479	581		
TB20	Carbon Nanotubes	480	Appendix D Mathematical Formulas		
10-5	Partial Fraction Expansion	483	585		
10-6	s-Domain Circuit-Element Models	489	Appendix E Answers to Selected Problems		
10-7	s-Domain Circuit Analysis	492	588		
10-8	Transfer Function and Impulse Response	497	Index		
10-9	Convolution Integral	498	591		
10-10	Multisim Analysis of Circuits Driven by Non-Trivial Inputs	506			