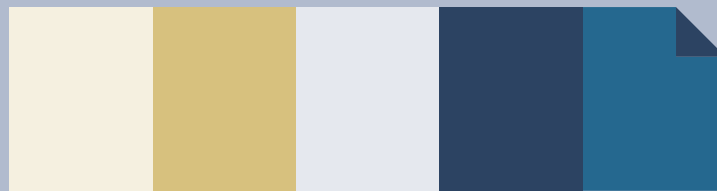


Chapter 1 Solutions **SAMPLE** for

CIRCUITS

Solutions for all problems and all chapters are provided in the full instructor solutions manual. This document provides a representative sample of the authors thoroughness and completeness. Only partial solutions for problems 1.1, 1.10, 1.14, and 1.25 are shown in this document.



Fawwaz T. Ulaby
The University of Michigan

Michel M. Maharbiz
The University of California, Berkeley



ISBN: 978-1-934891-00-1

Publisher: Tom Robbins
General Manager: Erik Luther
Marketing Manager: Brad Armstrong
Technology Manager : Mark Walters
Compositor: Paul Mailhot, PreTeX Inc.
Series Advisors: James H. McClellan, Georgia Institute of Technology
Charles G. Sodini, M.I.T.

Cover illustration: Courtesy of Canon U.S.A. All rights reserved.

©2009 National Technology and Science Press.

All rights reserved. Neither this book, nor any portion of it, may be copied or reproduced in any form or by any means without written permission of the publisher.

NTS Press respects the intellectual property of others, and we ask our readers to do the same. This book is protected by copyright and other intellectual property laws. Where the software referred to in this book may be used to reproduce software or other materials belonging to others, you should use such software only to reproduce materials that you may reproduce in accordance with the terms of any applicable license or other legal restriction.

LabVIEW, Multisim, and National Instruments are trademarks of National Instruments.

MATLAB® is a registered trademark of The MathWorks, Inc., 3 Apple Hill Drive, Natick, MA 01760-2098.

All other trademarks or product names are the property of their respective owners.

Library of Congress Cataloging-in-Publication Data Available

Additional Disclaimers:

The reader assumes all risk of use of this book and of all information, theories, and programs contained or described in it. This book may contain technical inaccuracies, typographical errors, other errors and omissions, and out-of-date information. Neither the author nor the publisher assumes any responsibility or liability for any errors or omissions of any kind, to update any information, or for any infringement of any patent or other intellectual property right.

Neither the author nor the publisher makes any warranties of any kind, including without limitation any warranty as to the sufficiency of the book or of any information, theories, or programs contained or described in it, and any warranty that use of any information, theories, or programs contained or described in the book will not infringe any patent or other intellectual property right. THIS BOOK IS PROVIDED "AS IS." ALL WARRANTIES, EITHER EXPRESS OR IMPLIED, INCLUDING, BUT NOT LIMITED TO, ANY AND ALL IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF INTELLECTUAL PROPERTY RIGHTS, ARE DISCLAIMED.

No right or license is granted by publisher or author under any patent or other intellectual property right, expressly, or by implication or estoppel.

IN NO EVENT SHALL THE PUBLISHER OR THE AUTHOR BE LIABLE FOR ANY DIRECT, INDIRECT, SPECIAL, INCIDENTAL, COVER, ECONOMIC, OR CONSEQUENTIAL DAMAGES ARISING OUT OF THIS BOOK OR ANY INFORMATION, THEORIES, OR PROGRAMS CONTAINED OR DESCRIBED IN IT, EVEN IF ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, AND EVEN IF CAUSED OR CONTRIBUTED TO BY THE NEGLIGENCE OF THE PUBLISHER, THE AUTHOR, OR OTHERS. Applicable law may not allow the exclusion or limitation of incidental or consequential damages, so the above limitation or exclusion may not apply to you.

CHAPTER 1

Sections 1-2 and 1-3: Dimensions, Charge, and Current

Problem 1.1 Use appropriate multiple and submultiple prefixes to express the following quantities:

- (a) 3,620 watts (W)
- (b) 0.000004 amps (A)
- (c) 5.2×10^{-6} ohms (Ω)
- (d) 3.9×10^{11} volts (V)
- (e) 0.02 meters (m)
- (f) 32×10^5 volts (V)

Solution:

- (a) $3,620 \text{ W} = 3.62 \text{ kW}$.
- (b) $0.000004 \text{ A} = 4 \mu\text{A}$.
- (c) $5.2 \times 10^{-6} \Omega = 5.2 \mu\Omega$.
- (d) Solution Hidden
- (e)
- (f)

Problem 1.10 Determine the net charge ΔQ that flowed through a certain device over the specified time intervals for each of the following currents:

- (a) $i(t) = [3t + 6t^3]$ mA, from $t = 0$ to $t = 4$ s
- (b) $i(t) = 4 \sin(40\pi t) \cos(40\pi t)$ μ A, from $t = 0$ to $t = 0.05$ s
- (c) $i(t) = [4e^{-t} - 3e^{-2t}]$ A, from $t = 0$ to $t = \infty$
- (d) $i(t) = 12e^{-3t} \cos(40\pi t)$ nA, from $t = 0$ to $t = 0.05$ s

Solution:

(a)

$$\begin{aligned} \Delta Q(0, 4) &= \int_0^4 i dt = \left[\int_0^4 (3t + 6t^3) dt \times 10^{-3} \right] \\ &= \left(\frac{3t^2}{2} + \frac{6t^4}{4} \right) \Big|_0^4 \times 10^{-3} = 408 \quad (\text{mC}). \end{aligned}$$

(b)

$$\begin{aligned} \Delta Q(0, 0.05) &= \int_0^{0.05} i dt = \left[\int_0^{0.05} 4 \sin 40\pi t \cos 40\pi t dt \right] \times 10^{-6} \\ &= \frac{4}{2 \times 40\pi} \sin^2 40\pi t \Big|_0^{0.05} \times 10^{-6} = 0. \end{aligned}$$

(c)

$$\Delta Q(0, \infty) = \int_0^{\infty} i dt = \int_0^{\infty} (4e^{-t} - 3e^{-2t}) dt = \left(-4e^{-t} + \frac{3}{2}e^{-2t} \right) \Big|_0^{\infty} = 2.5 \quad (\text{C}).$$

(d)

$$\Delta Q(0, 0.05) = \int_0^{0.05} i dt = \left[\int_0^{0.05} 12e^{-3t} \cos 40\pi t dt \right] \times 10^{-9}.$$

From Tables of Integrals,

$$\int e^{ax} \cos bx dx = e^{ax} \frac{(a \cos bx + b \sin bx)}{a^2 + b^2}.$$

Hence,

Solution Hidden

Problem 1.14 Given that the current in mA flowing through a wire is given by


$$i(t) = \begin{cases} 0, & \text{for } t < 0, \\ 6t, & \text{for } 0 \leq t \leq 5 \text{ s}, \\ 30e^{-0.6(t-5)}, & \text{for } t \geq 5 \text{ s}, \end{cases}$$

(a) Sketch $i(t)$ versus t .

(b) Sketch $q(t)$ versus t .

Solution:

(a)

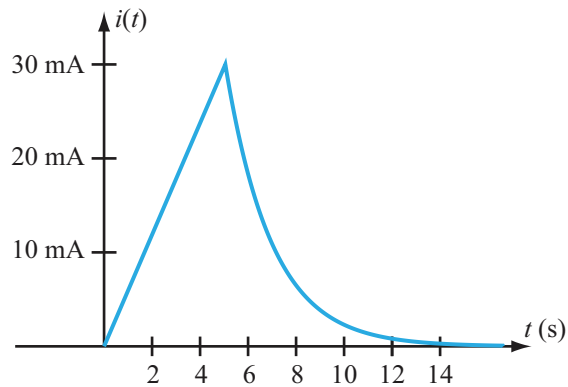


(b) $q(t) = \int_{-\infty}^t i(t) dt$.

For $0 \leq t \leq 5$ s,

$$q(t) = \left(\int_0^t 6t dt \right) \text{Solution Hidden} \text{ (mC)}.$$

For $t \geq 5$ s,

$$\begin{aligned} q(t) &= \left[\int_0^5 6t dt + \int_5^t 30e^{-0.6(t-5)} dt \right] \times 10^{-3} \\ &= \left[\frac{6t^2}{2} \Big|_0^5 + 30e^{+3} \int_5^t e^{-0.6t} dt \right] \times 10^{-3} \\ &= \text{Solution Hidden} \text{ (mC)}. \end{aligned}$$

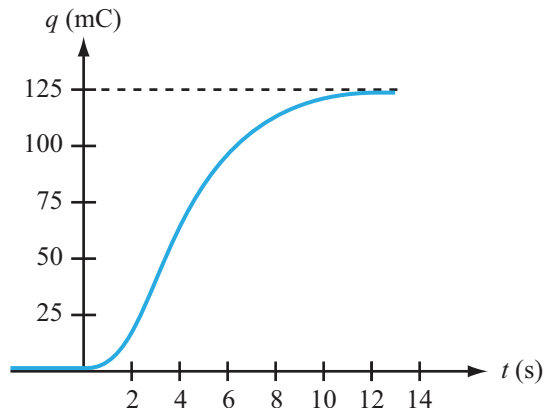

Problem 1.25 For the circuit in Fig. P1.25, generate circuit diagrams that include only those elements that have current flowing through them for

- (a) $t < 0$
- (b) $0 < t < 2 \text{ s}$
- (c) $t > 2 \text{ s}$


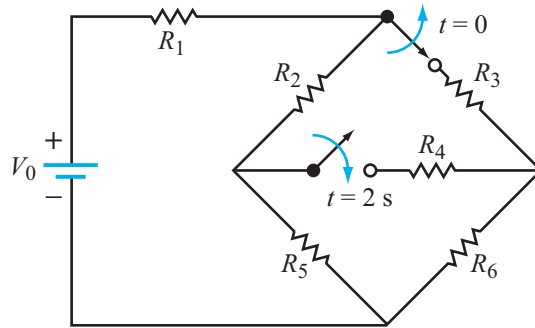



Figure P1.25: Circuit for Problem 1.25.

Solution:

(a) $t < 0$

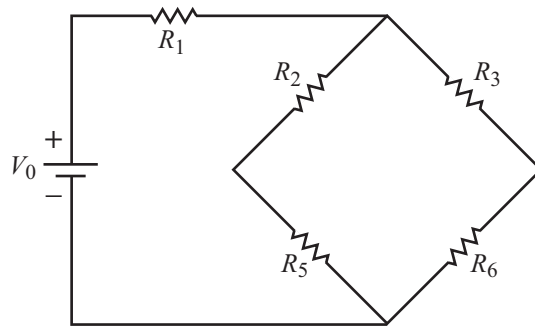

(b) $0 < t < 2 \text{ s}$

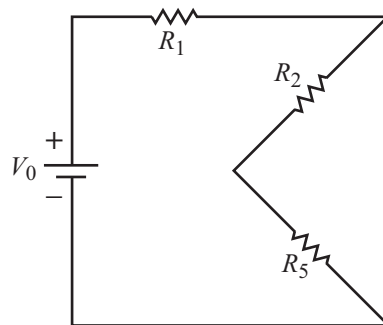

(c) Solution Hidden